

ISTANBUL TECHNICAL UNIVERSITY
COMPUTER ENGINEERING DEPARTMENT

BLG 222E
COMPUTER ORGANIZATION
PROJECT 3

EXPERIMENT NO : 3
EXPERIMENT DATE : 03.06.2020
GROUP NO : G18

GROUP MEMBERS:

150160141 : RESUL LEVENT KURU
150170043 : EBRAR ÖMER
150180064 : MELİS GÜNŞEBER
150180715 : GÖKSU GÜZ

SPRING 2020

Contents

FRONT COVER

CONTENTS

| | | |
|----------|-----------------------------------------------------------------------------------------------------------------------------|----------|
| 1 | INTRODUCTION | 1 |
| 2 | ORGANIZATION | 1 |
| 2.1 | Instructions | 1 |
| 2.1.1 | Fetch and Decode | 1 |
| | T0:IR(8-15) \leftarrow M[PC] | 1 |
| | T1:PC \leftarrow PC + 1 | 1 |
| | T2:IR(0-7) \leftarrow M[PC] | 1 |
| | T3:PC \leftarrow PC + 1 | 2 |
| 2.1.2 | Execute | 2 |
| | <u>D0: Ri \leftarrow Value</u> | 2 |
| | IR(8)=1(Direct) | 2 |
| | IR(8)=0(Immediate) | 2 |
| | <u>D1: Value \leftarrow R_i - 2</u> | |
| | <u>D2: Destreg \leftarrow SrcReg1</u> | 3 |
| | <u>D3: M[SP] \leftarrow SrcReg1, SP \leftarrow SP - 1</u> | 4 |
| | <u>D4: SP \leftarrow SP + 1, DestReg \leftarrow M[SP]</u> | 5 |
| | <u>D5: Destreg \leftarrow SrcReg1 + SrcReg2</u> | 5 |
| | <u>D6: Destreg \leftarrow SrcReg1 - SrcReg2</u> | 8 |
| | <u>D7: DestReg \leftarrow Destreg-1</u> | 11 |
| | <u>D8: DestReg \leftarrow Destreg+1</u> | 11 |
| | <u>D9: Destreg \leftarrow Srcreg1 and SrcReg2</u> | 12 |
| | <u>D10: Destreg \leftarrow Srcreg1 OR Srcreg2</u> | 14 |
| | <u>D11: Destreg \leftarrow NOT Srcreg1</u> | 17 |
| | <u>D12: Destreg \leftarrow LSL Srcreg1</u> | 18 |
| | <u>D13: Destreg \leftarrow LSR Srcreg1</u> | 19 |
| | <u>D14: PC \leftarrow Value</u> | 20 |
| | <u>D15: If Z = 1 then PC \leftarrow Value</u> | 20 |
| | <u>D16: If Z = 0 then PC \leftarrow Value</u> | 20 |
| | <u>D17: M[SP] \leftarrow PC, SP \leftarrow SP - 1, PC \leftarrow Value</u> | 21 |
| | <u>D18: SP \leftarrow SP + 1, PC \leftarrow M[SP]</u> | 21 |
| 2.2 | Implementations | 22 |

| | | |
|--------|------------------------------------|----|
| 2.2.1 | Instruction | 22 |
| 2.2.2 | Decoding Opcode | 23 |
| 2.2.3 | Time | 24 |
| 2.2.4 | Sequence Counter | 25 |
| 2.2.5 | Read and load | 25 |
| 2.2.6 | Clock L/H Input Z enable | 26 |
| 2.2.7 | Funsels | 27 |
| 2.2.8 | Mux Selections | 29 |
| 2.2.9 | OutSelections | 31 |
| 2.2.10 | Register Selections | 33 |
| 2.2.11 | Control unit | 35 |

3 CONCLUSION 35

1 INTRODUCTION

In this project we are asked to design a control unit which produce control signals. Computer has instructions to make operations which are fetch, decoded and executed.

2 ORGANIZATION

The control unit performs operations at three stages within specific times.

2.1 Instructions

2.1.1 Fetch and Decode

T0:IR(8-15) \leftarrow M[PC] At first, we select the PC at OutDsel and send it to memory to read what is in the PC.

OutDsel: 00;
Read: 1;
L/H':0;
Enable: 1;
FunselT:01

T1:PC \leftarrow PC + 1 Then, we increment the program counter to read the operation part of IR.

RegselP2B: 001;
FunselP2B: 10;

T2:IR(0-7) \leftarrow M[PC] We read the IR but not the address part and decide to operation.

OutDsel: 00;
Read: 1;
L/H':1;
Enable: 1;
FunselT:01

T3:PC \leftarrow **PC** + 1 The fetch operation ends after that time, the operation starts with the decoded opcode.

RegselP2B: 001;

FunselP2B: 10;

2.1.2 Execute

D0: Ri \leftarrow **Value** We write the value to the register that choosen.

IR(8)=1(Direct) D0T4:

MuxBSel: 01;

RegSelP2B: 010;

FunSelP2B: 01;

D0T5:

OutDSel: 01;

Read: 1;

MuxASel: 01;

RegSelP2A: IR(10,9));

FunselP2A: 01;

SC < - 0;

IR(8)=0(Immediate) D0T4:

MuxASel: 00;

RegSelP2A: IR(10,9));

FunSelP2A: 01;

SC < - 0;

D1: Value \leftarrow **R_i** With this operation we can store the value from a register.

D1T4:

MuxBSel: 01;

RegSelP2B: 010;

FunselP2B: 01;

D1T5:

OutDSel: 01;
OutASel: IR(10,9);
MuxCSel: 1;
FunSelALU: 0000;
Load: 1
SC < - 0;

D2: Destreg \leftarrow SrcReg1 This instruction moves data between the registers.

IR10'IR7': (Reg. file \leftarrow Reg. File)

D2T4:

OutASel: IR(6,5);
MuxCSel:1
FunSelALU: 0000;
MuxASel: 11;
RegSelP2B: IR(9,8);
FunSelP2B: 01;
SC < - 0;

IR10'IR7': (Reg. file \leftarrow Add. Reg. File)

D2T4:

OutCSel: IR(6,5);
MuxASel: 10;
RegSelP2B: IR(9,8);
FunSelX: 01;
SC < - 0;

IR10IR7': (Add. Reg. file \leftarrow Reg. File)

D2T4:

OutASel: IR(6,5);
MuxCSel: 1;
FunSelALU: 0000;
MuxBSel: 11;
RegSelP2A: IR(9,8);
FunSelY: 01;

SC \leftarrow 0;

IR10IR7: (Reg. file \leftarrow Add. Reg. File)

D2T4:

OutASel: IR(6,5);

MuxASel: 10;

RegSelP2A: IR(9,8);

FunSelY: 01;

SC \leftarrow 0;

D3: M[SP] \leftarrow SrcReg1, SP \leftarrow SP - 1 Data in register will be stored in stack register, and stack pointer will be decreased.

IR7: (data from Address Register File)

D3T4:

OutDSel: 01;

OutCSel: IR(6,5);

MuxASel: 10;

MuxCsel=0;

FunselAlu=0000;

Load: 1;

IR7': (data from Register File) D3T4:

OutASel: Ir(6,5);

MuxCsel=1;

FunSelALU: 0000;

Load: 1;

T5 Common

D3T5:

RegSelP2b: 100;

FunSelp2b: 10;

SC \leftarrow 0;

D4: $\text{SP} \leftarrow \text{SP} + 1$, $\text{DestReg} \leftarrow \text{M}[\text{SP}]$ Data will be pushed from stack register and written Source Register.

D4T4:

RegselP2B: 100;

FunSelP2B: 10;

IR10: (Source register is Address Register File)

D4T5:

OutDSel: 11;

Read : 1;

MuxBSel: 10;

RegSelP2A: IR(9,8);

FunSelP2A: 01;

SC \leftarrow 0;

IR10': (Source register is Register File)

D4T5:

OutDSel: 11;

Read : 1;

MuxASel: 01;

RegSelP2B: IR(9,8);

FunSelY: 01;

SC \leftarrow 0;

D5: $\text{Destreg} \leftarrow \text{SrcReg1} + \text{SrcReg2}$ Data from the source registers will be added and written in destination register.

IR10'IR7'IR4': (reg. file \leftarrow reg. file + reg. file)

D5T4:

OutASel: IR(6,5);

MuxCSel: 1;

OutBSel: IR(3,2);

MuxDSel: 0;

FunSelALU: 0100;

MuxASel: 11;

RegSelP2A: IR(9,8);

FunSelP2A: 01;

SC \leftarrow 0;

IR10'IR7'IR4: (reg. file \leftarrow reg. file + address reg. file)

D5T4:

OutASel: IR(6,5);

MuxCSel: 1;

OutDSel: IR(3,2);

MuxDSel: 1;

FunSelALU: 0100;

MuxASel: 11;

RegSelP2A: IR(9,8);

FunSelP2A: 01;

SC \leftarrow 0;

IR10'IR7 IR4': (reg. file \leftarrow address reg. file + reg. file)

D5T4:

OutCSel: IR(6,5);

MuxCSel: 1;

OutDSel: IR(3,2);

MuxDSel: 0;

FunSelALU: 0100;

MuxASel: 11;

RegSelP2A: IR(9,8);

FunSelP2A: 01;

SC \leftarrow 0;

IR10'IR7 IR4: (reg. file \leftarrow address reg. file + address reg. file)

D5T4:

OutCSel: IR(6,5);

MuxCSel: 0;

OutBSel: IR(3,2);

MuxDSel: 0;

FunSelALU: 0100;

MuxASel: 11;

RegSelP2A: IR(9,8);

FunSelP2A: 01;

SC \leftarrow 0;

IR10 IR7' IR4': (address reg. file \leftarrow reg. file + reg. file)

D5T4:

OutASel: IR(6,5);

MuxCSel: 1;

OutBSel: IR(3,2);

MuxDSel: 0;

FunSelALU: 0100;

MuxBSel: 11;

RegSelP2B: IR(9,8);

FunSelP2B: 01;

SC \leftarrow 0;

IR10 IR7' IR4: (address reg. file \leftarrow reg. file + address reg. file)

D5T4:

OutASel: IR(6,5);

MuxCSel: 1;

OutDSel: IR(3,2);

MuxDSel: 1;

FunSelALU: 0100;

MuxBSel: 11;

RegSelP2B: IR(9,8);

FunSelP2B: 01;

SC \leftarrow 0;

IR10 IR7 IR4': (address reg. file \leftarrow address reg. file + reg. file)

D5T4:

OutCSel: IR(6,5);

MuxCSel: 0;

OutBSel: IR(3,2);

MuxDSel: 0;

FunSelALU: 0100;

MuxBSel: 11;

RegSelP2B: IR(9,8);

FunSelP2B: 01;

SC \leftarrow 0;

IR10 IR7 IR4: (address reg. file \leftarrow address reg. file + address reg. file)

D5T4:

OutCSel: IR(6,5);

MuxCSel: 0;

OutDSel: IR(3,2);

MuxDSel: 1;

FunSelALU: 0100;

MuxBSel: 11;

RegSelP2B: IR(9,8);

FunSelP2B: 01;

SC \leftarrow 0;

D6: Destreg \leftarrow SrcReg1 - SrcReg2 Data will be subtracted between the source registers and written in destination register.

IR10'IR7'IR4': (reg. file \leftarrow reg. file - reg. file)

D6T4:

OutASel: IR(6,5);

MuxCSel: 1;

OutBSel: IR(3,2);

MuxDSel: 0;

FunSelALU: 0110;

MuxASel: 11;

RegSelP2A: IR(9,8);

FunSelP2A: 01;

SC \leftarrow 0;

IR10'IR7'IR4: (reg. file \leftarrow reg. file - address reg. file)

D6T4:

OutASel: IR(6,5);

MuxCSel: 1;

OutDSel: IR(3,2);

MuxDSel: 1;

FunSelALU: 0110;

MuxASel: 11;
RegSelP2A: IR(9,8);
FunSelP2A: 01;
SC \leftarrow 0;

IR10'IR7 IR4': (reg. file \leftarrow address reg. file - reg. file)

D6T4:

OutCSel: IR(6,5);
MuxCSel: 0;
OutBSel: IR(3,2);
MuxDSel: 0;
FunSelALU: 0110;
MuxASel: 11;
RegSelP2A: IR(9,8);
FunSelP2A: 01;
SC \leftarrow 0;

IR10'IR7 IR4: (reg. file \leftarrow address reg. file - address reg. file)

D6T4:

OutCSel: IR(6,5);
MuxCSel: 0;
OutDSel: IR(3,2);
MuxDSel: 0;
FunSelALU: 0110;
MuxASel: 11;
RegSelP2A: IR(9,8);
FunSelP2A: 01;
SC \leftarrow 0;

IR10 IR7' IR4': (address reg. file \leftarrow reg. file - reg. file)

D6T4:

OutASel: IR(6,5);
MuxCSel: 1;
OutBSel: IR(3,2);
MuxDSel: 0;
FunSelALU: 0110;
MuxBSel: 11;

RegSelP2B: IR(9,8);
FunSelP2B: 01;
SC \leftarrow 0;

IR10 IR7' IR4: (address reg. file \leftarrow reg. file - address reg. file)

D6T4:

OutASel: IR(6,5);
MuxCSel: 1;
OutDSel: IR(3,2);
MuxDSel: 1;
FunSelALU: 0110;
MuxBSel: 11;
RegSelP2B: IR(9,8);
FunSelP2B: 01;
SC \leftarrow 0;

IR10 IR7 IR4': (address reg. file \leftarrow address reg. file - reg. file)

D6T4:

OutCSel: IR(6,5);
MuxCSel: 0;
OutBSel: IR(3,2);
MuxDSel: 0;
FunSelALU: 0110;
MuxBSel: 11;
RegSelP2B: IR(9,8);
FunSelP2B: 01;
SC \leftarrow 0;

IR10 IR7 IR4: (address reg. file \leftarrow address reg. file - address reg. file)

D6T4:

OutCSel: IR(6,5);
MuxCSel: 0;
OutDSel: IR(3,2);
MuxDSel: 1;
FunSelALU: 0110;
MuxBSel: 11;
RegSelP2B: IR(9,8);

FunSelP2B: 01;
SC \leftarrow 0;

D7: DestReg \leftarrow Destreg-1 Data in the destination register will be decremented by 1 and written again in destination register

IR10: (Source register is Address Register File)

D7T4:

RegSelP2B: IR(9.8);
FunSelP2B: 11;
SC \leftarrow 0;

IR10': (Source register is Register File)

D7T4:

RegSelP2A: IR(9.8);
FunSelP2A: 11;
SC \leftarrow 0;

D8: DestReg \leftarrow Destreg+1 Data in the destination register will be incremented by 1 and written again in destination register

IR10: (Source register is Address Register File)

D8T4:

RegSelP2B: IR(9.8);
FunSelP2B: 10;
SC \leftarrow 0;

IR10': (Source register is Register File)

D8T4:

RegSelP2A: IR(9.8);
FunSelP2A: 10;
SC \leftarrow 0;

D9: Destreg \leftarrow Srcreg1 and SrcReg2 IR10' IR7' IR4'(Register File \leftarrow Register File) In this operation register sources will be compared by and operation and the result will be given to the destination register.

D9T4:

OutASel:IR(6,5); MuxCSel: 1;

OutBSel: IR(3,2);

MuxDSel: 0;

FunSelAlu: 0111

MuxASel: 11;

RegSelP2A: IR(9,8);

FunSelP2A: 01;

SC \leftarrow 0;

IR10' IR7' IR4(Register File \leftarrow Register File and Address Register File)

D9T4:

OutDSel:IR(6,5); MuxCSel: 1;

OutCSel: IR(3,2);

MuxDSel: 1;

FunSelAlu: 0111

MuxASel: 11;

RegSelP2A: IR(9,8);

FunSelP2A: 01;

SC \leftarrow 0;

IR10' IR7 IR4'(Register File \leftarrow Register File and Address Register File)

D9T4:

OutDSel:IR(6,5); MuxCSel: 1;

OutBSel: IR(3,2);

MuxDSel: 0;

FunSelAlu: 0111

MuxASel: 11;

RegSelP2A: IR(9,8);

FunSelP2A: 01;

SC \leftarrow 0;

IR10' IR7 IR4(Register File←Address Register File and Address Register File)

D9T4:

OutDSel:IR(6,5); MuxCSel: 1;

OutCSel: IR(3,2);

MuxDSel: 1;

FunSelAlu: 0111

MuxASel: 11;

RegSelP2A: IR(9,8);

FunSelP2A: 01;

SC←0;

IR10 IR7' IR4'(Address Register File←Register File and Register File)

D9T4:

OutASel:IR(6,5); MuxCSel: 1;

OutBSel: IR(3,2);

MuxDSel: 1;

FunSelAlu: 0111

MuxBSel: 11;

RegSelP2B: IR(9,8);

FunSelP2B: 01;

SC←0;

IR10 IR7' IR4(Address Register File←Register File and Address Register File)

D9T4:

OutASel:IR(6,5); MuxCSel: 1;

OutCSel: IR(3,2);

MuxDSel: 1;

FunSelAlu: 0111

MuxBSel: 11;

RegSelP2B: IR(9,8);

FunSelP2B: 01;

SC←0;

IR10 IR7 IR4'(Address Register File← Address Register File and Register File)

D9T4:

OutDSel:IR(6,5); MuxCSel: 1;
OutBSel: IR(3,2);
MuxDSel: 1;
FunSelAlu: 0111
MuxBSel: 11;
RegSelP2B: IR(9,8);
FunSelP2B: 01;
SC←0;

IR10 IR7 IR4(Address Register File← Address Register File and Address Register File)

D9T4:

OutDSel:IR(6,5); MuxCSel: 1;
OutCSel: IR(3,2);
MuxDSel: 1;
FunSelAlu: 0111
MuxBSel: 11;
RegSelP2B: IR(9,8);
FunSelP2B: 01;
SC←0;

D10: Destreg ←Srcreg1 OR Srcreg2 IR10' IR7' IR4'(Reg File←Not Register File)

In this operation, two source registers bit will be operated by or function then the result given to the destination register.

D10T4:

OutASel:IR(6,5); MuxCSel: 1;
OutBSel: IR(3,2);
MuxDSel: 0;
FunSelALU: 1000;
MuxASel: 11;
RegSelP2A: IR(9,8)
FunSelP2A: 01;
SC←0;

IR10' IR7' IR4(Register File← Register File or Address Register File)

D10T4:

OutASel:IR(6,5); MuxCSel: 1;
OutCSel: IR(3,2);
MuxDSel: 1;
FunSelALU: 1000;
MuxASel: 11;
RegSelP2A: IR(9,8)
FunSelP2A: 01;
SC←0;

IR10' IR7 IR4'(Register File← Address Register File or Register File)

D10T4:

OutDSel:IR(6,5); MuxASel: 10;
MuxCSel: 0;
OutBSel: IR(3,2);
MuxDSel: 0;
FunSelALU: 1000;
MuxASel: 11;
RegSelP2A: IR(9,8)
FunSelP2A: 01;
SC←0;

IR10' IR7 IR4(Register File← Address Register File or Address Register File)

D10T4:

OutDSel:IR(6,5); MuxASel: 10;
MuxCSel: 0;
OutCSel: IR(3,2);
MuxDSel: 1;
FunSelALU: 1000;
MuxASel: 11;
RegSelP2A: IR(9,8)
FunSelP2A: 01;
SC←0;

IR10 IR7' IR4'(Address Register File← Register File or Register File)

D10T4:

OutASel:IR(6,5); MuxCSel: 1;

OutBSel: IR(3,2);
MuxDSel: 0;
FunSelALU: 1000;
MuxBSel: 11;
RegSelP2B: IR(9,8)
FunSelP2B: 01;
SC←0;

IR10 IR7' IR4(Address Register File← Register File or Address Register File)

D10T4:

OutASel:IR(6,5); MuxCSel: 1;
OutCSel: IR(3,2);
MuxDSel: 1;
FunSelALU: 1000;
MuxBSel: 11;
RegSelP2B: IR(9,8)
FunSelP2B: 01;
SC←0;

IR10 IR7 IR4'(Address Register File←Address Register File or Register File)

D10T4:

OutDSel:IR(6,5); MuxASel: 10;
MuxCSel: 0;
OutCSel: IR(3,2);
MuxDSel: 1;
FunSelALU: 1000;
MuxBSel: 11;
RegSelP2B: IR(9,8)
FunSelP2B: 01;
SC←0;

IR10 IR7 IR4(Address Register File← Register File or Address Register File)

D10T4:

OutASel:IR(6,5); MuxASel: 10;
MuxCSel: 0;
OutBSel: IR(3,2);
MuxDSel: 1;

FunSelALU: 1000;
MuxBSel: 11;
RegSelP2B: IR(9,8)
FunSelP2B: 01;
SC←0;

D11: Destreg ← NOT Srcreg1 IR10' IR7'(Register File←Not Register File)

Source Register will be invert into its Not self then written to the destination register.

D11T4:

OutASel:IR(6,5); MuxCSel: 1;
FunSelALU: 0010;
MuxASel: 11;
RegSelP2A: IR(9,8)
FunSelP2A: 01;
SC←0;

IR10' IR7'(Reg File←Not Address Register File)

D11T4:

OutDSel:IR(6,5); MuxASel: 10;
MuxCSel: 0;
FunSelAlu: 0010;
MuxASel: 11;
RegSelP2A: IR(9,8);
FunSelP2A: 01;
SC←0;

IR10 IR7'(Reg File←Not Address Register File)

D11T4:

OutDSel:IR(6,5); MuxCSel: 1;
FunSelAlu: 0010;
MuxASel: 11;
RegSelP2B: IR(9,8);
FunSelP2B: 01;
SC←0;

IR10 IR7(Reg File←Not Address Register File)

D11T4:

OutDSel:IR(6,5); MuxASel: 10;
MuxCSel: 0;
FunSelAlu: 0010;
MuxASel: 11;
RegSelP2B: IR(9,8);
FunSelP2B: 01;
SC←0;

D12: Destreg ← LSL Srcreg1 IR10' IR7'(Reg File←Not Register File)

Source Register 1 will be shifted left and written to the destination register.

D12T4:

OutASel:IR(6,5); MuxCSel: 1;
FunSelALU: 1010;
MuxASel: 11;
RegSelP2A: IR(9,8)
FunSelP2A: 01;
SC←0;

IR10' IR7'(Reg File←Not Address Register File)

D12T4:

OutDSel:IR(6,5); MuxASel: 10;
MuxCSel: 0;
FunSelAlu: 1010;
MuxASel: 11;
RegSelP2A: IR(9,8);
SC←0;

IR10 IR7'(Address Register File←Not Register File)

D12T4:

OutASel:IR(6,5); MuxCSel: 1;
FunSelAlu: 1010;
MuxBSel: 11;
RegSelP2B: IR(9,8);
FunSelP2B: 01;
SC←0;

IR10 IR7(Address Register File←Not Register File)D12T4:

OutASel:IR(6,5); MuxASel: 10;

FunSelAlu: 1010;

MuxBSel: 11;

RegSelP2B: IR(9,8);

FunSelP2B: 01;

SC←0;

D13: Destreg ← LSR Srcreg1

Source Register 1 will be shifted right and written to the destination register.

IR10' IR7'(Address Register File←Not Register File)D13T4:

OutASel:IR(6,5); MuxCSel: 1;

FunSelALU: 1011;

MuxASel: 11;

RegSelP2A: IR(9,8)

FunSelP2A: 01;

SC←0;

IR10' IR7(Reg File←Not Address Register File)D13T4:

OutDSel:IR(6,5); MuxASel: 10;

MuxCSel: 0;

FunSelAlu: 1011;

MuxASel: 11;

RegSelP2A: IR(9,8);

SC←0;

IR10 IR7'(Address Register File←Not Register File)D13T4:

OutASel:IR(6,5); MuxCSel: 1;

FunSelAlu: 1011;

MuxBSel: 11;

RegSelP2B: IR(9,8);

FunSelP2B: 01;
SC \leftarrow 0;

IR10 IR7(Address Register File \leftarrow Not Register File)

D13T4:

OutASel:IR(6,5); MuxASel: 10;
FunSelAlu: 1011;
MuxBSel: 11;
RegSelP2B: IR(9,8);
FunSelP2B: 01;
SC \leftarrow 0;

D14: PC \leftarrow Value We write the value to PC.

D14T4:

MuxBSel:01;
RegSelP2B: 001;
FunSelP2B: 01;
SC \leftarrow 0;

D15: If Z = 1 then PC \leftarrow Value We write the value to PC for condition Z = 1.

Z': SC \leftarrow 0;
Z: D15T4:
MuxBSel:01;
RegSelP2B: 001;
FunSelP2B: 01;
SC \leftarrow 0;

D16: If Z = 0 then PC \leftarrow Value We write the value to PC for condition Z = 0.

Z: SC \leftarrow 0;
Z': D16T4:
MuxBSel:01;
RegSelP2B: 001;
FunSelP2B: 01;

SC \leftarrow 0;

D17: M[SP] \leftarrow PC, SP \leftarrow SP - 1, PC \leftarrow Value

D17T4:

OutDSel:11;

OutCSel:00;

MuxASel:10;

MuxCSel:0;

FunSelAlu:0001;

Load: 1

D17T5:

RegSelP2B: 100;

FunSelP2B: 11;

D17T6:

RegSelP2B:001;

FunSelP2B: 01;

SC \leftarrow 0;

D18: SP \leftarrow SP + 1, PC \leftarrow M[SP]

D18T4:

RegSelP2B: 100;

FunSelP2B: 10;

D18T5:

OutDSel:10;

Load: 1

MuxBSel:10;


RegSelP2B:001;

FunSelP2B: 01;


SC \leftarrow 0;

2.2 Implementations


2.2.1 Instruction

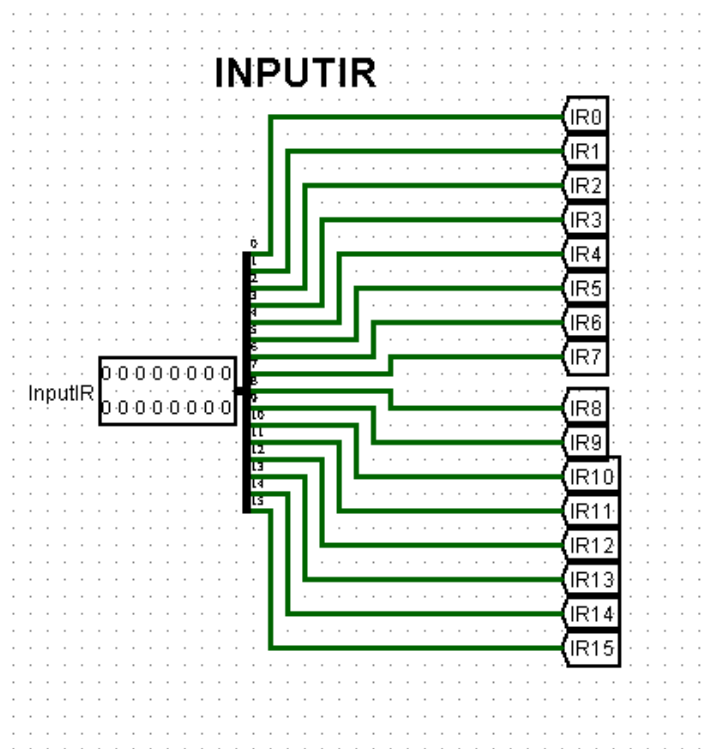


2.2.2 Decoding Opcode

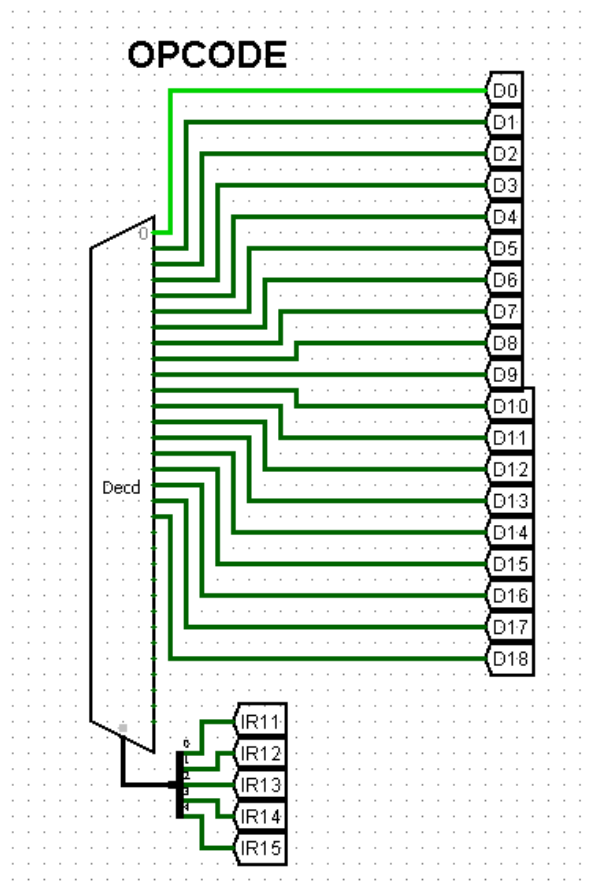


2.2.3 Time

 


2.2.4 Sequence Counter




 


2.2.5 Read and load

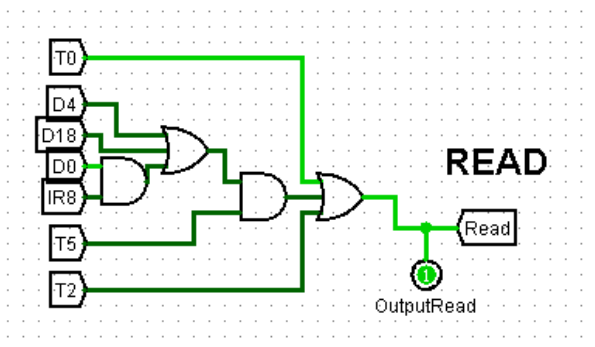



 



2.2.6 Clock L/H Input Z enable

    


2.2.7 Funsels

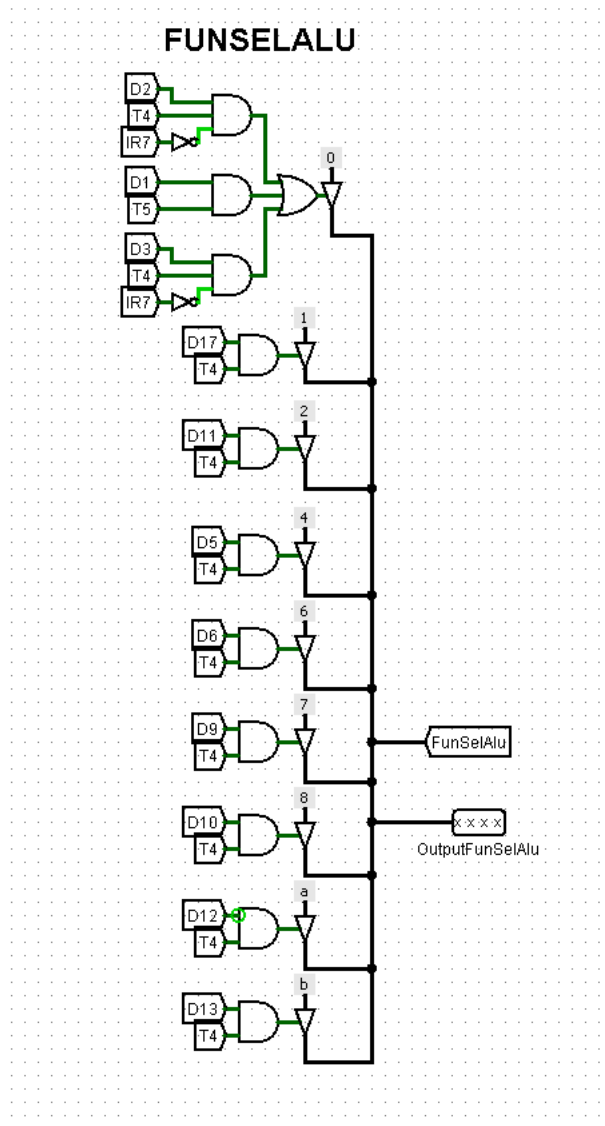


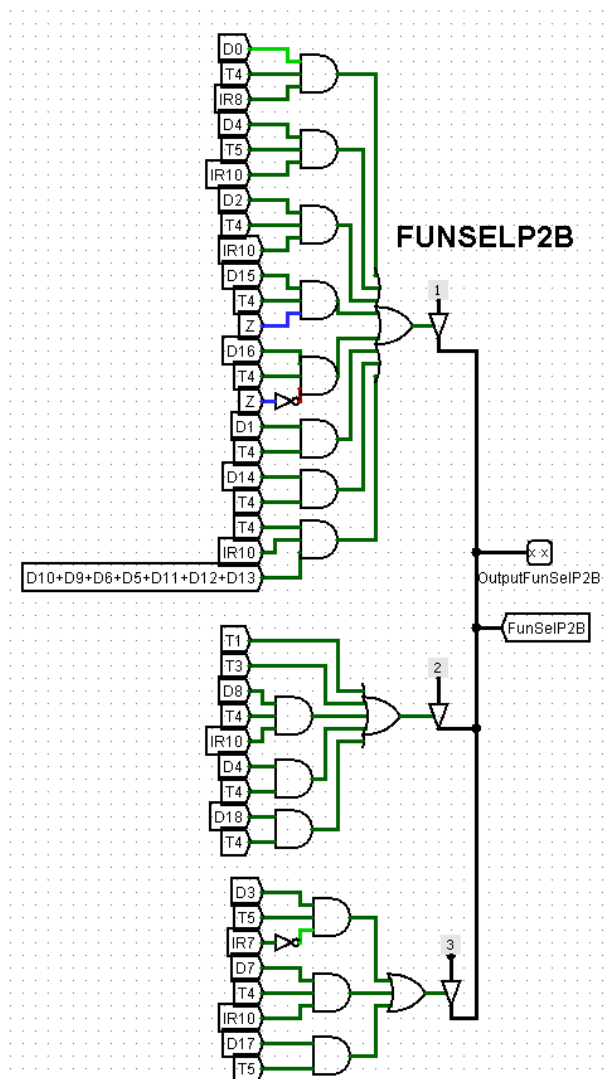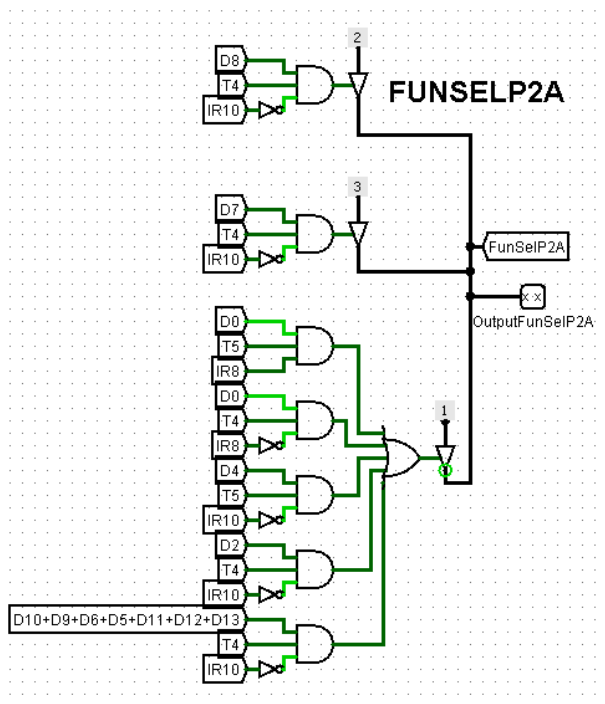


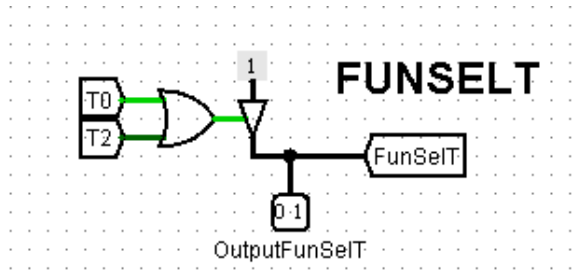


2.2.8 Mux Selections



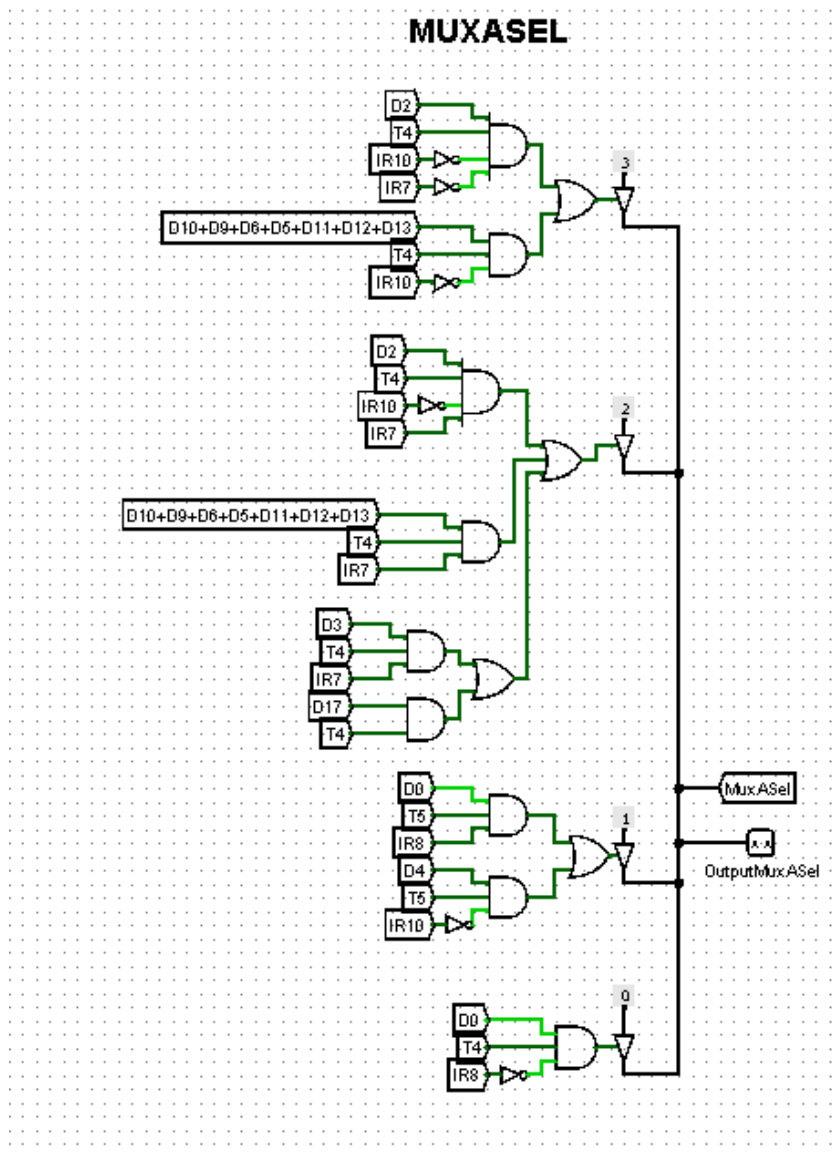


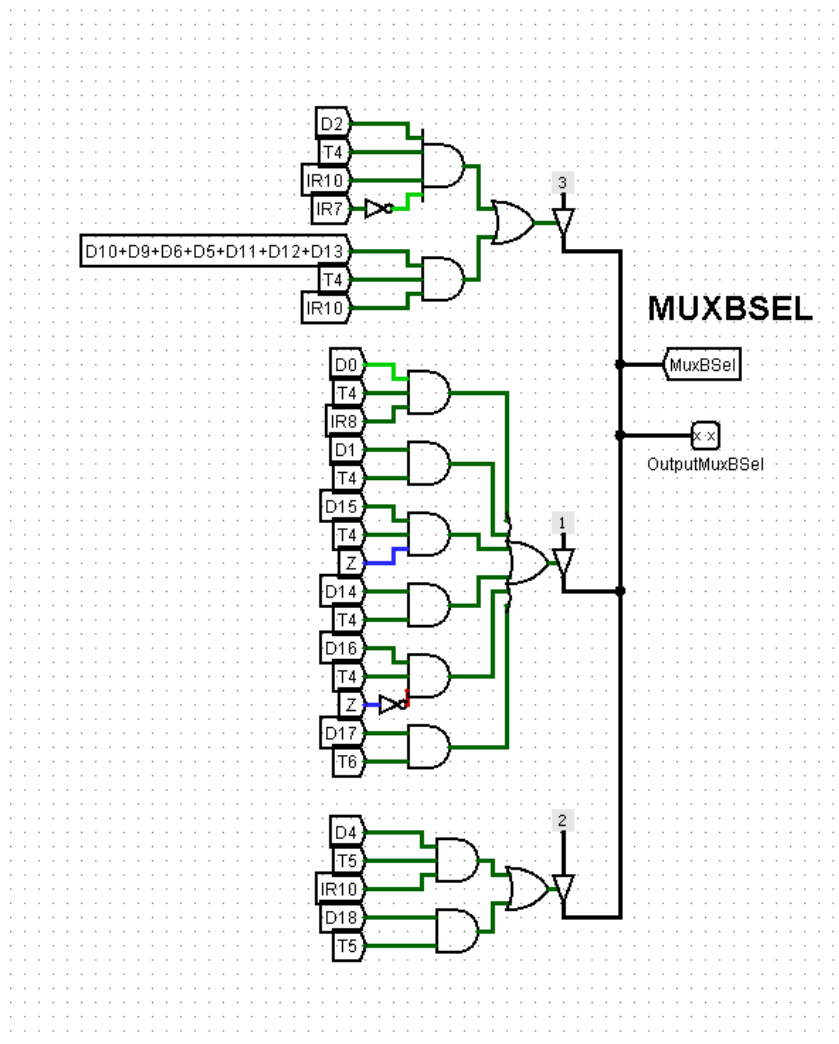


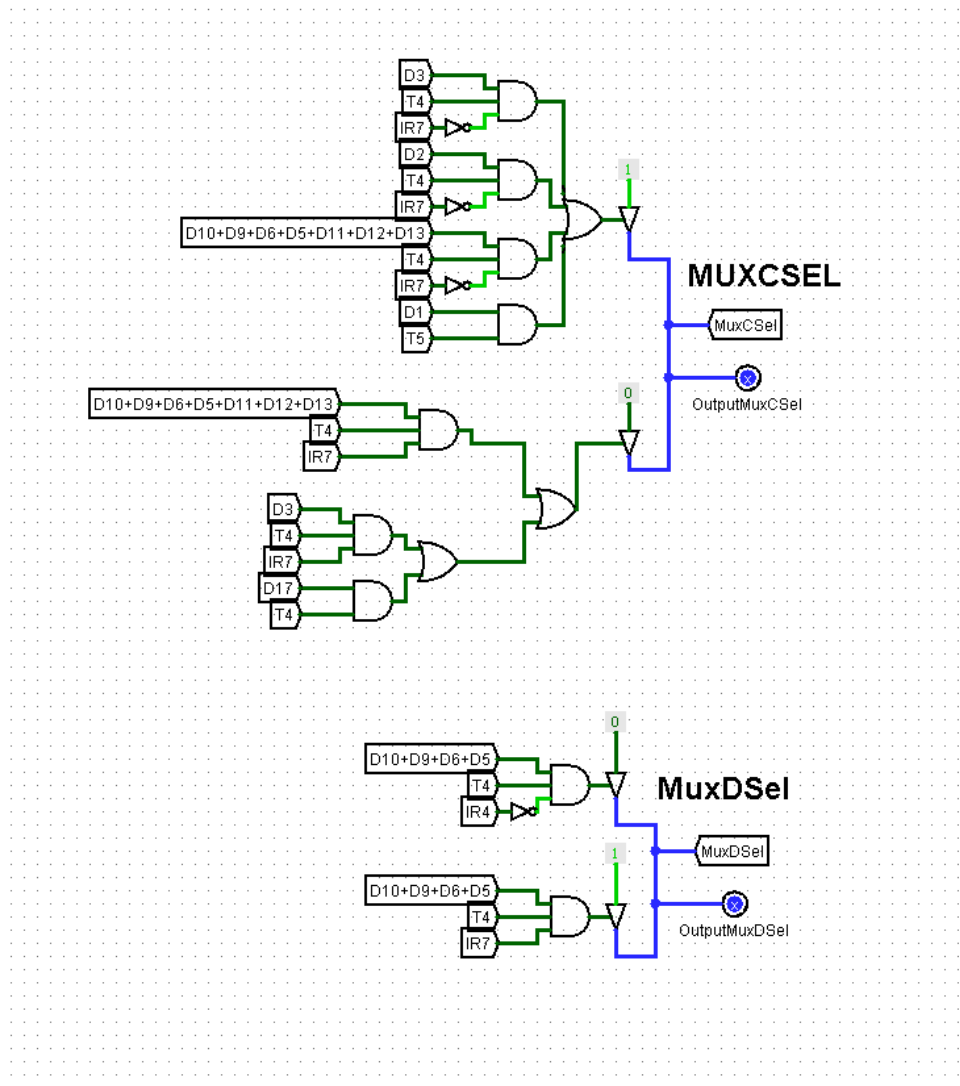



2.2.9 OutSelections

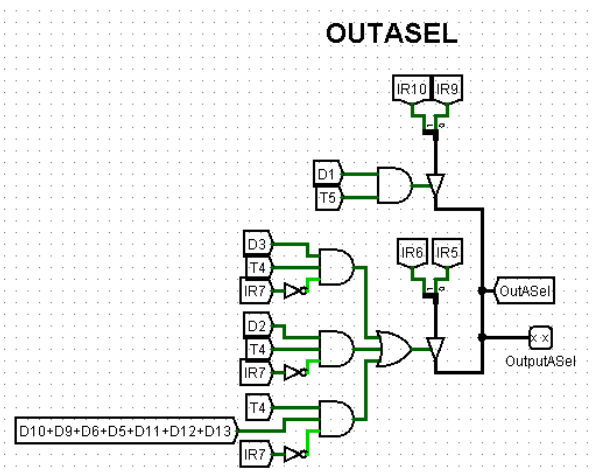

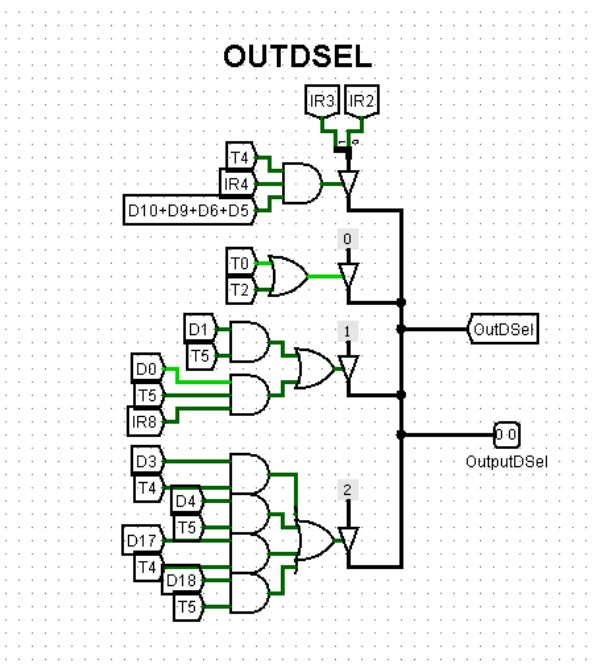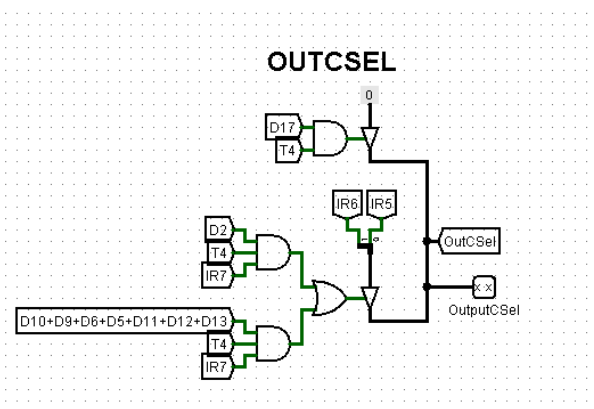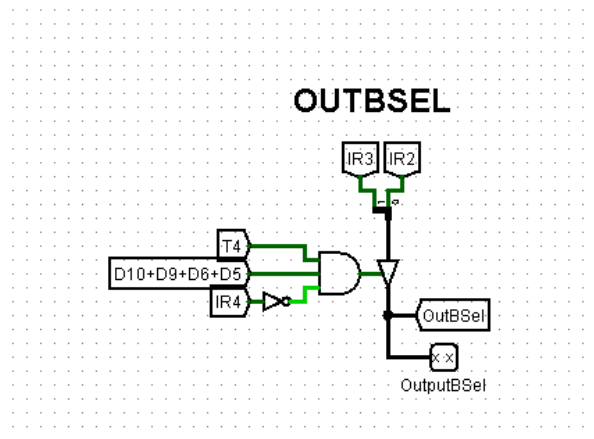


2.2.10 Register Selections

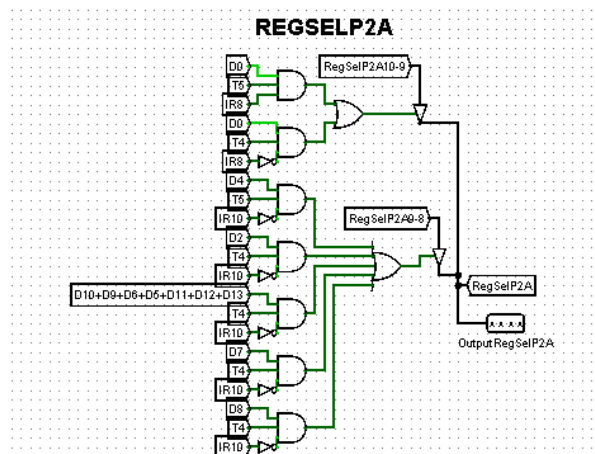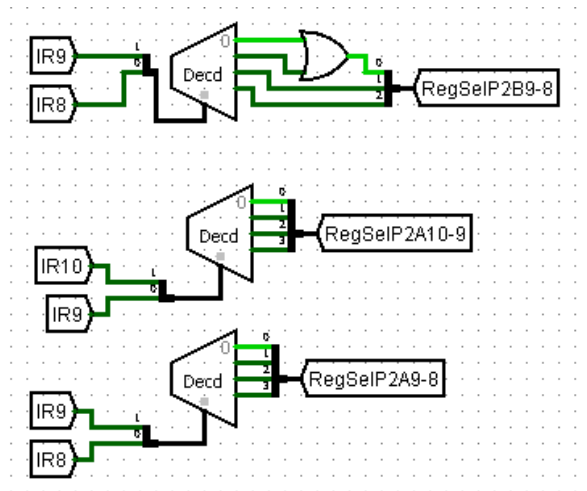

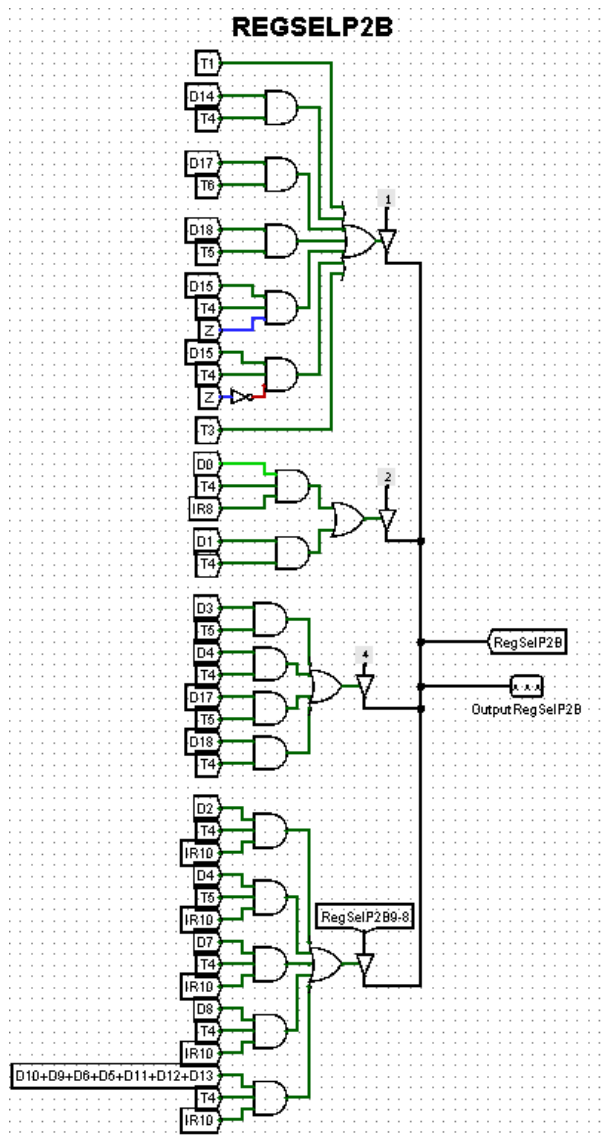

2.2.11 Control unit

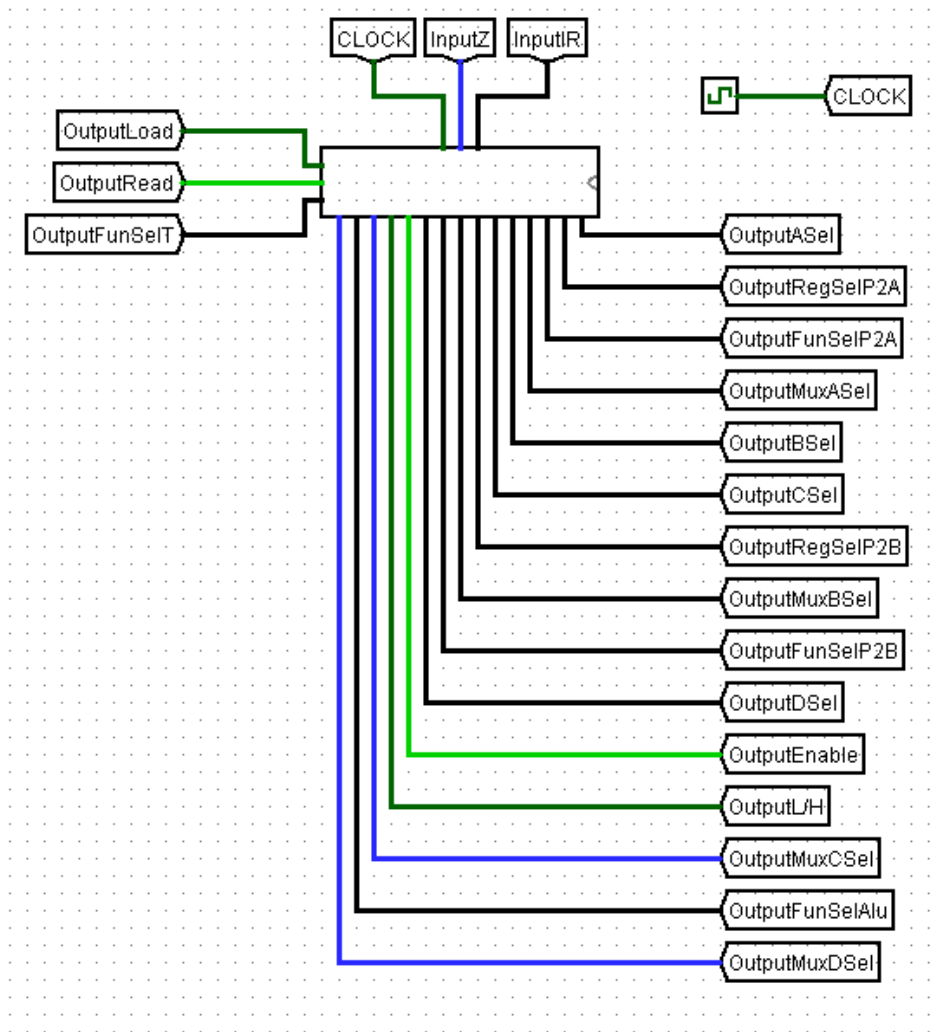

3 CONCLUSION

In this project we were asked to design a basic computer which has the functionalities that we were given in the project. Designing this project, we learned the basic functionalities and the structure of a computer. It was hard to understand those operations at first, but with the required researches we finally understood the mechanism, and implemented it.